

worksheet 7.6.3 page 1

$R_g := 4.7 \ \Omega$        $R_L := 10^7 \ \Omega$       Impedances of source and load

$V_{meas} := 0.41 \ \text{V}$       Measured voltage between horizontal sections of square wave

$C_{rad} := 220 \cdot 10^{-12} \ \text{F}$       Value assigned to radiation capacitor. Adjust to suit

$R_{cable} := 1 \ \Omega$       Resistor which simulates cable losses. Adjust to suit

$R_{o1} := 50 \ \Omega$      $R_{o2} := R_{o1}$      $R_{o3} := 600 \ \Omega$     See figure 6.6.1. **Adjust to suit**

$Loss := \frac{R_{o2}}{R_{o2} + R_{o3}}$       Equation (6.6.3)

$R_o := R_{o1} + \frac{R_{o2} \cdot R_{o3}}{R_{o2} + R_{o3}} = 96.154$       Equation (6.6.1)

$Z_T := 2.27 \ \Omega$       See equation (7.2.6)

$K := \frac{50}{96.2}$       See equation (7.6.1)

$V_g := \frac{V_{meas}}{K}$        $V_g = 0.789$       See equation (6.6.11)

$T := 83 \cdot 10^{-9} \ \text{s}$       Measured transit time. Adjust to suit

$N := 100$       Number of time-steps per transit

$dt := \frac{T}{N}$       Time of each step

$T_1 := 120 \cdot 10^{-9} \ \text{s}$       Time of leading edge of square wave, as displayed on oscilloscope

$T_2 := 1.65 \cdot 10^{-6} \ \text{s}$       Time of trailing edge of square wave, as displayed on oscilloscope

$T_3 := 2 \cdot 10^{-6} \ \text{s}$       Sweep time of oscilloscope

$N_1 := \frac{T_1}{dt}$        $N_2 := \frac{T_2}{dt}$        $N_3 := \frac{T_3}{dt}$       Number of time steps at which each event occurs.

$n := 1 .. N_3$        $t_n := (n - 1) \cdot dt$       Definition of horizontal axis of display

Figure 6.6.2 Definition of input variables.

```

recv (INPUT) :=      Ifi ← INPUTi
                      Ifa ←  $\frac{2 \cdot R_o \cdot I_{fi}}{R_L + R_o}$ 
                      Ifr ← Ifa - Ifi
                       $\begin{pmatrix} \text{Ifa} \\ \text{Ifr} \end{pmatrix}$ 

```

Copy of function defined in figure 6.4.4

worksheet 7.6.3 page 3

point(n) :=  $\begin{cases} m \leftarrow \text{mod}(n, N) \\ m \leftarrow N \text{ if } m = 0 \end{cases}$

Vch1 :=  $\begin{array}{l} \text{data}_{2,N} \leftarrow 0 \\ \text{near}_5 \leftarrow 0 \\ \text{for } i \in 1..N3 \\ \quad \begin{array}{l} \text{Vgen} \leftarrow \text{Vg if } i > N1 \\ \text{Vgen} \leftarrow 0 \text{ if } i > N2 \\ p \leftarrow \text{point}(i) \\ \text{INPUT} \leftarrow \text{data}^{\langle p \rangle} \\ \text{near} \leftarrow \text{send}(\text{near}, \text{INPUT}, \text{Vgen}) \\ \left( \begin{array}{c} \text{Ina} \\ \text{Int} \\ \text{Ine} \\ \text{Ins} \\ \text{Qns} \end{array} \right) \leftarrow \text{near} \\ \left( \begin{array}{c} \text{Ifa} \\ \text{Ifr} \end{array} \right) \leftarrow \text{recv}(\text{INPUT}) \\ \text{OUTPUT} \leftarrow \left( \begin{array}{c} \text{Int} \\ \text{Ifr} \end{array} \right) \\ \text{data}^{\langle p \rangle} \leftarrow \text{OUTPUT} \\ \text{Idiff} \leftarrow \text{Ina} - \text{Ine} \\ \text{Vin} \leftarrow \text{Vgen} - \text{Rg} \cdot (\text{Ina} + \text{Ins}) \\ \text{Vch1} \leftarrow \text{K} \cdot \text{Vin} \\ \text{Vdiff} \leftarrow \text{ZT} \cdot \text{Idiff} \\ \text{Vrad} \leftarrow \text{ZT} \cdot \text{Ine} \\ \text{Vi} \leftarrow \text{Vrad} \end{array} \end{array}$

equation (6.6.9)

equation (6.6.10)

equation (6.6.11)

equation (6.6.12)

equation (6.6.12)

V

channel 1 selected as output variable

Figure 6.6.4 Main routine used to analyse transient response.(page 3 of worksheet)

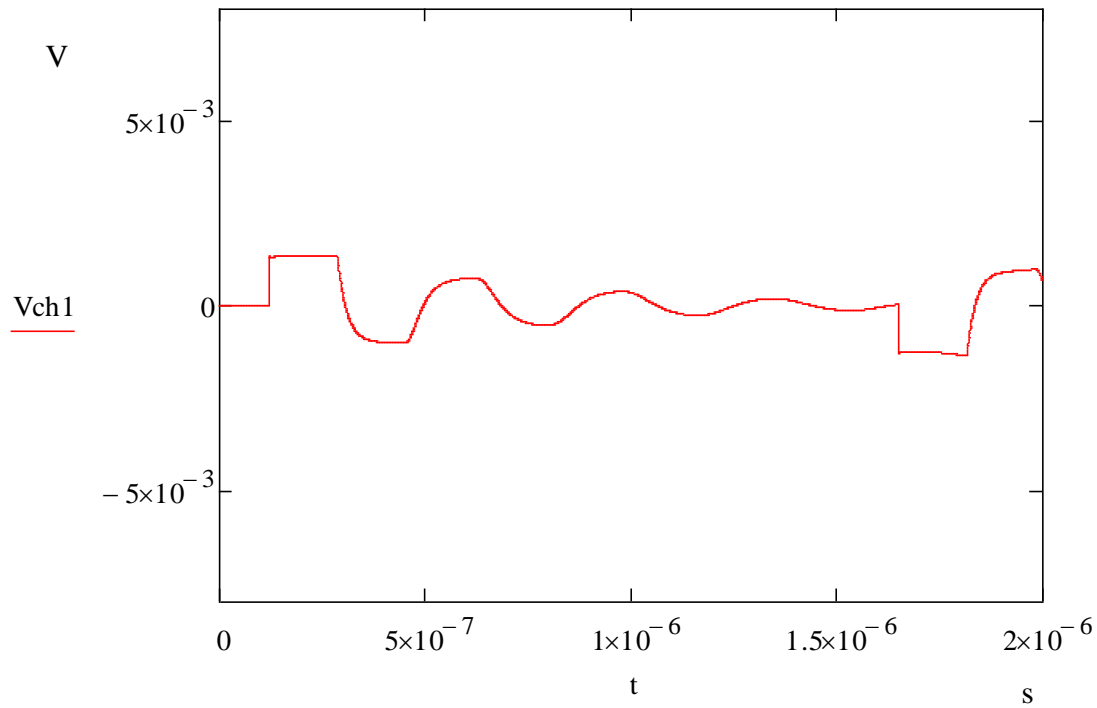


Figure 7.6.8 Simulated voltage at channel 2 input. Antenna current monitored

$$T1 = 1.2 \times 10^{-7} \quad T2 = 1.65 \times 10^{-6} \quad T3 = 2 \times 10^{-6} \quad Crad = 2.2 \times 10^{-10}$$

$$Ro1 = 50 \quad Ro3 = 600 \quad Loss = 0.077 \quad Ro = 96.154 \quad Rcable = 1$$

$$V_{meas} = 0.41$$

Vertical scale: top = 8 mV, bottom = -8 mV

Horizontal scale : 2 micro-seconds