

Worksheet 6.1.2

$$R1 := 5000 \quad \Omega$$

$$R2 := 20 \quad \Omega$$

$$R3 := 10^6 \quad \Omega$$

$$L1 := 1 \cdot 10^{-3} \quad \text{H}$$

$$C1 := 100 \cdot 10^{-9} \quad \text{F}$$

$$V_{\text{gen}} := 1 \quad \text{V}$$

$$\text{dt} := 10^{-8} \quad \text{s}$$

$$D := \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

$$\text{next}(D) := \left| \begin{array}{l} I2 \leftarrow D_2 \\ I3 \leftarrow D_3 \\ Q \leftarrow D_4 \\ I1 \leftarrow \frac{1}{R1 + R2} \cdot \left(V_{\text{gen}} + R2 \cdot I2 - \frac{Q}{C1} \right) \\ I2 \leftarrow \frac{1}{R2 + R3} \cdot \left(R2 \cdot I1 + R3 \cdot I3 + \frac{Q}{C1} \right) \\ dI3 \leftarrow \frac{dt}{L1} \cdot R3 \cdot (I2 - I3) \\ I3 \leftarrow I3 + dI3 \\ Q \leftarrow Q + (I1 - I2) \cdot dt \\ \begin{pmatrix} I1 \\ I2 \\ I3 \\ Q \end{pmatrix} \end{array} \right.$$

$$T := 100 \cdot 10^{-6} \quad \text{s}$$

$$N := \text{ceil} \left(\frac{T}{dt} \right)$$

$$i := 2 \dots N$$

$$I_{\text{out}_i} := \left| \begin{array}{l} D \leftarrow \text{next}(D) \\ D_3 \end{array} \right.$$

$$t_i := (i - 1) \cdot dt$$

Figure 6.1.5 Calculating the waveform of the current in 1 mH inductor

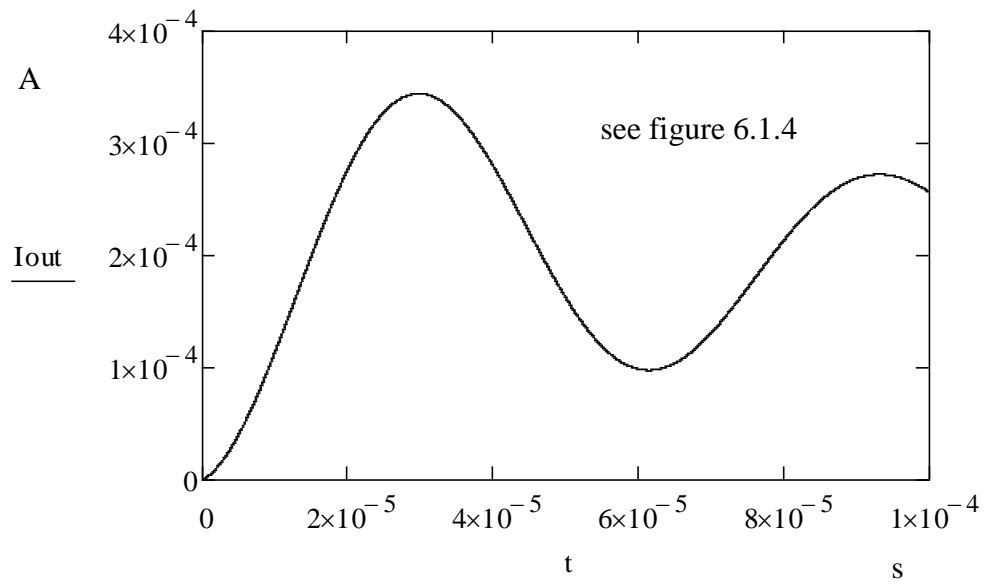


Figure 6.1.6 Waveform of the current in the inductor of the parallel LCR circuit

$$\frac{1}{2 \cdot \pi \cdot \sqrt{L1 \cdot C1}} = 1.592 \times 10^4 \qquad 2 \cdot \pi \cdot \sqrt{L1 \cdot C1} = 6.283 \times 10^{-5}$$

$$\sqrt{\frac{L1}{C1}} = 100$$