

data :=	(	0.005	8	98	<p>column 1: frequency, MHz  column 2: channel 1 voltage, V  column 3: channel 2 voltage, mV</p>
		0.01	8	175	
		0.02	8	270	
		0.05	8	340	
		0.1	8	360	
		0.2	8	365	
		0.5	8	375	
		1	8	370	
		2	8	370	
		5	7.9	365	
		10	7.8	360	
		15	7.4	335	
		19	6.9	330	
		)			

$s_s := 1 \dots \text{rows}(\text{data})$	$f_s := \text{data}_{s,1} \cdot 10^6$										
$ZT_s :=$	<table border="0"> <tr><td style="border-left: 1px solid black; padding-left: 5px;">Vch1</td><td><math>\leftarrow \text{data}_{s,2}</math></td></tr> <tr><td style="border-left: 1px solid black; padding-left: 5px;">Vch2</td><td><math>\leftarrow \text{data}_{s,3} \cdot 10^{-3}</math></td></tr> <tr><td style="border-left: 1px solid black; padding-left: 5px;">Iprim</td><td><math>\leftarrow \frac{Vch1}{50}</math></td></tr> <tr><td style="border-left: 1px solid black; padding-left: 5px;"></td><td></td></tr> <tr><td style="border-left: 1px solid black; padding-left: 5px;"><math>\frac{Vch2}{Iprim}</math></td><td></td></tr> </table>	Vch1	$\leftarrow \text{data}_{s,2}$	Vch2	$\leftarrow \text{data}_{s,3} \cdot 10^{-3}$	Iprim	$\leftarrow \frac{Vch1}{50}$			$\frac{Vch2}{Iprim}$	
Vch1	$\leftarrow \text{data}_{s,2}$										
Vch2	$\leftarrow \text{data}_{s,3} \cdot 10^{-3}$										
Iprim	$\leftarrow \frac{Vch1}{50}$										
$\frac{Vch2}{Iprim}$											

Fig 7.2.6 Using the test results to calculate the transfer impedance

worksheet 7.2 page 2

$$y1 := \log(5 \cdot 10^3)$$

$$y2 := \log(20 \cdot 10^6)$$

Calculating a set of 100 frequencies,  
equally spaced between 5 kHz  
and 20 MHz.

$$m := \frac{y2 - y1}{100}$$

$$i := 1..101$$

$$F_i := \left| \begin{array}{l} y \leftarrow m \cdot (i - 1) + y1 \\ 10^y \end{array} \right.$$

$$R1 := 300 \ \Omega$$

$$R2 := 51 \ \Omega$$

$$R3 := 50 \ \Omega$$

$$R4 := 850 \ \Omega$$

$$L1 := 200 \cdot 10^{-6} \text{ H}$$

$$C1 := 60 \cdot 10^{-12} \text{ F}$$

$$\text{Turns} := 10$$

$$ZT_m := \left| \begin{array}{l} \omega \leftarrow 2 \cdot \pi \cdot F_i \\ Z1 \leftarrow R4 + \frac{1}{j \cdot \omega \cdot C1} \\ Y2 \leftarrow \frac{1}{R1} + \frac{1}{R2} + \frac{1}{R3} + \frac{1}{j \cdot \omega \cdot L1} + \frac{1}{Z1} \\ Z2 \leftarrow \frac{1}{Y2} \\ ZT \leftarrow \frac{|Z2|}{\text{Turns}} \end{array} \right.$$

Figure 7.2.8 Calculating the transfer impedance of the circuit model

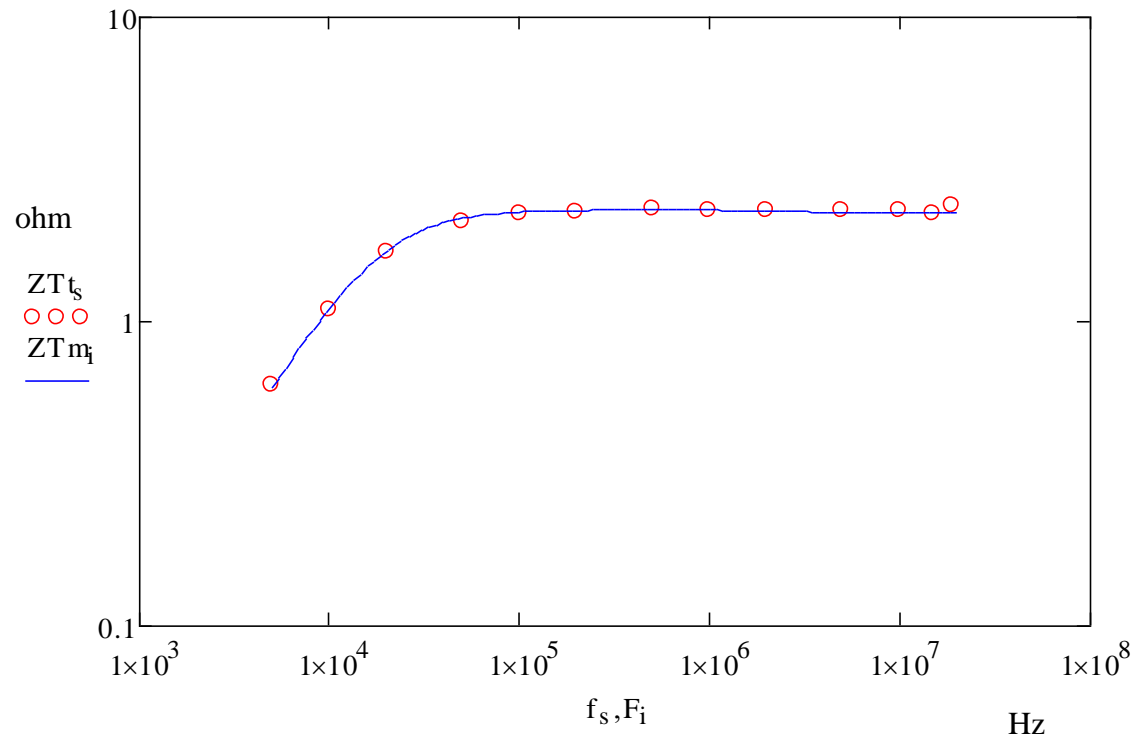


Figure 7.2.9 Transfer impedance from test results,  $ZT_t$ , and from circuit model,  $ZT_m$