

Worksheet 7.6.4

From the waveform of figure 7.6.2, the amplitude of the step voltage measured by channel 1, at the end of the first exponential rise, is:

$$V_{ch1} := 0.39 \cdot V$$

The voltage applied to the input terminals of the line is related to V_{ch1} by equation (7.6.1)

$$V_{in} := \frac{96.2}{50} \cdot V_{ch1} = 0.75 \text{ V}$$

From the waveform of figure 7.6.5, the voltage measured by channel 2 is:

$$V_{ch2} := 0.016 \cdot V$$

The ratio of the amplitude of V_{ch2} to the amplitude of the current monitored by the current transformer is given by equation (7.2.6)

$$R_T := 2.27 \cdot \Omega$$

Invoking equation (7.2.5) $I_{out} := \frac{V_{ch2}}{R_T} = 7.048 \times 10^{-3} \text{ A}$

The ratio of V_{in} to I_{out} gives a measure of the characteristic impedance of the cable:

$$R_o := \frac{V_{in}}{I_{out}} = 106 \Omega$$

The waveform of figure 7.6.5 also gives a measure of the time taken for a current step to propagate to the far end and return to the near end. This is the time difference between the first and second edges of the waveform. This gives:

$$T := \frac{166 \cdot 10^{-9}}{2} \cdot \text{sec}$$

The capacitance and inductance of the cable can be determined by invoking equations (6.3.7) and (6.3.6)

$$C_a := \frac{T}{R_o} = 7.8 \times 10^{-10} \text{ F}$$

$$L_a := T \cdot R_o = 8.8 \times 10^{-6} \text{ H}$$

These results can be compared with those obtained from cable characterisation tests. From figure 7.5.12.

$$C_{a_} := 2 \cdot \frac{1}{2} \cdot 929 \cdot \text{pF} = 9.29 \times 10^{-10} \text{ F}$$

$$L_{a_} := 8 \cdot 1.05 \mu\text{H} = 8.4 \times 10^{-6} \text{ H}$$

Figure 7.6.9 Calculating values of components derived for 15 m cable, using data from transient tests and frequency response tests