

worksheet 6.2 page 1

see figure 6.2.1

$$R_o := 100 \ \Omega$$

$$R_g := 10 \ \Omega$$

$$R_L := 1000 \ \Omega$$

$$V_{gen} := 10 \text{ V}$$

$$T := 100 \cdot 10^{-9} \text{ s}$$

$$N1 := 100$$

$$\Delta t := \frac{T}{N1}$$

$$N2 := 30 \cdot N1$$

$$\text{send}(\text{INPUT}, V_{gen}) := \begin{cases} \text{Ini} \leftarrow \text{INPUT}_2 \\ \text{Ina} \leftarrow \frac{2 \cdot R_o \cdot \text{Ini} + V_{gen}}{R_g + R_o} \\ \text{Inr} \leftarrow \text{Ina} - \text{Ini} \\ \begin{pmatrix} \text{Ina} \\ \text{Inr} \end{pmatrix} \end{cases}$$

$$\text{recv}(\text{INPUT}) := \begin{cases} \text{Ifi} \leftarrow \text{INPUT}_1 \\ \text{Ifa} \leftarrow \frac{2 \cdot R_o \cdot \text{Ifi}}{R_L + R_o} \\ \text{Ifr} \leftarrow \text{Ifa} - \text{Ifi} \\ \begin{pmatrix} \text{Ifa} \\ \text{Ifr} \end{pmatrix} \end{cases}$$

$$\text{point}(n) := \begin{cases} m \leftarrow \text{mod}(n, N1) \\ m \leftarrow N1 \text{ if } m = 0 \end{cases}$$

$$\text{Ina} := \begin{cases} \text{data2}_{,N1} \leftarrow 0 \\ \text{for } i \in 1 \dots N2 \\ \quad \begin{cases} p \leftarrow \text{point}(i) \\ \text{INPUT} \leftarrow \text{data}^{\langle p \rangle} \\ \begin{pmatrix} \text{Ina} \\ \text{Inr} \end{pmatrix} \leftarrow \text{send}(\text{INPUT}, V_{gen}) \\ \begin{pmatrix} \text{Ifa} \\ \text{Ifr} \end{pmatrix} \leftarrow \text{recv}(\text{INPUT}) \\ \text{OUTPUT} \leftarrow \begin{pmatrix} \text{Inr} \\ \text{Ifr} \end{pmatrix} \\ \text{data}^{\langle p \rangle} \leftarrow \text{OUTPUT} \\ I_i \leftarrow \text{Ina} \end{cases} \end{cases} \\ I \end{cases}$$

$$n := 1 \dots N2 \quad t_n := (n - 1) \cdot \Delta t$$

Figure 6.2.5 Calculating the waveform of the current at the near end of the line

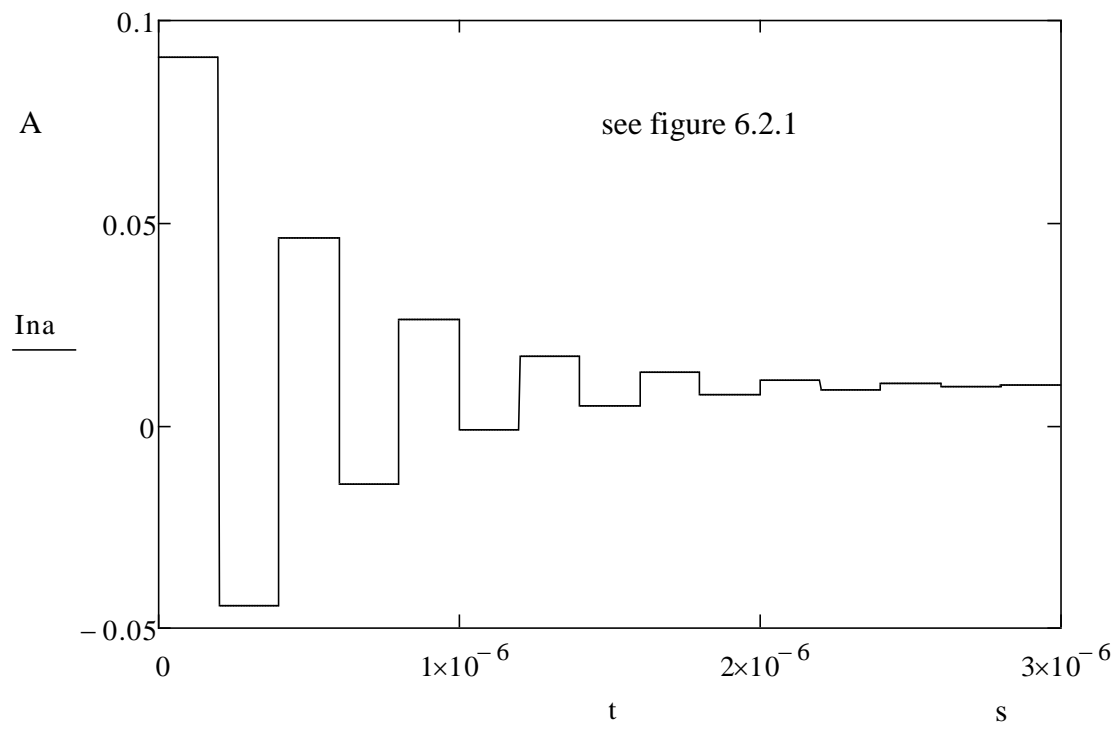


Figure 6.2.6 Waveform of the current delivered to input of transmission line